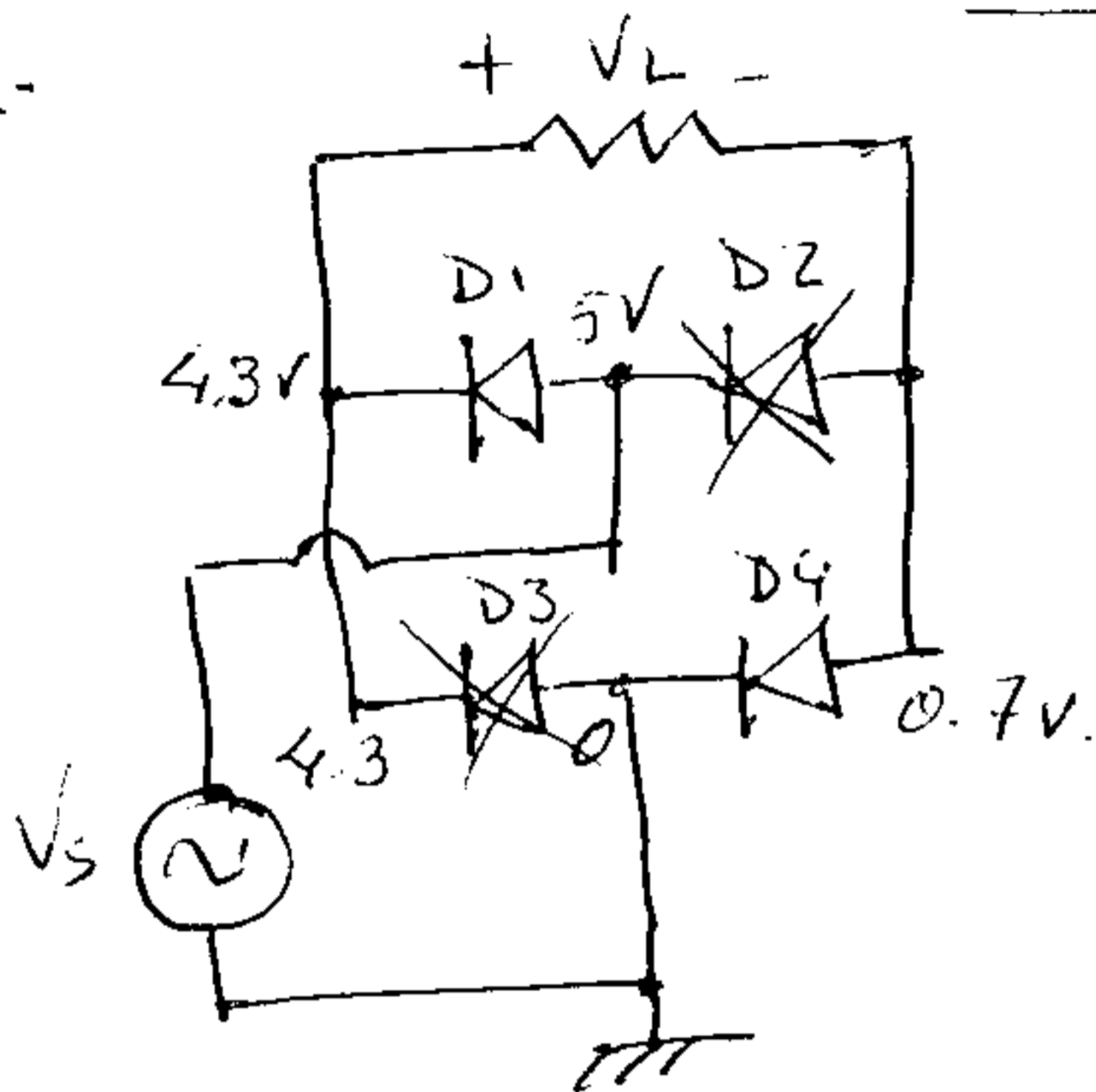


MIC 4120
EXAMEN INTRA 24 FEVR 2010

SOLUTIONS


Q1.-



a) D1, D4 sont ON
D2, D3 OFF $V_s = 5V$

$$I = \frac{4.3 - 0.7}{R_L} = \frac{3.6}{R_L}$$


$$V_L = 3.6V$$

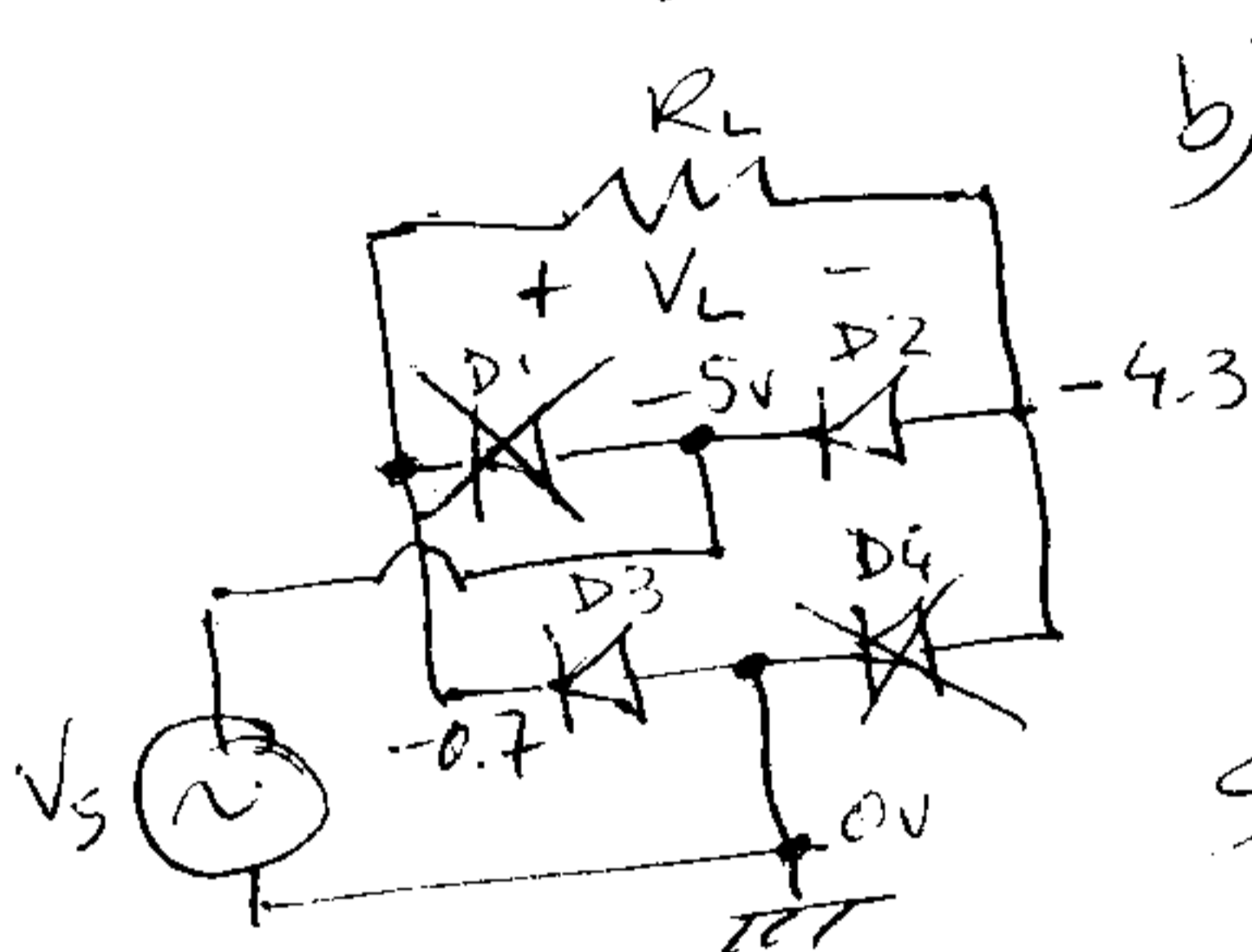

b) $V_s = -5V$
D2, D3 ON
D1, D4 OFF

$$I = \frac{-4.3 + 0.7}{R_L}$$

$$V_L = 3.6V$$

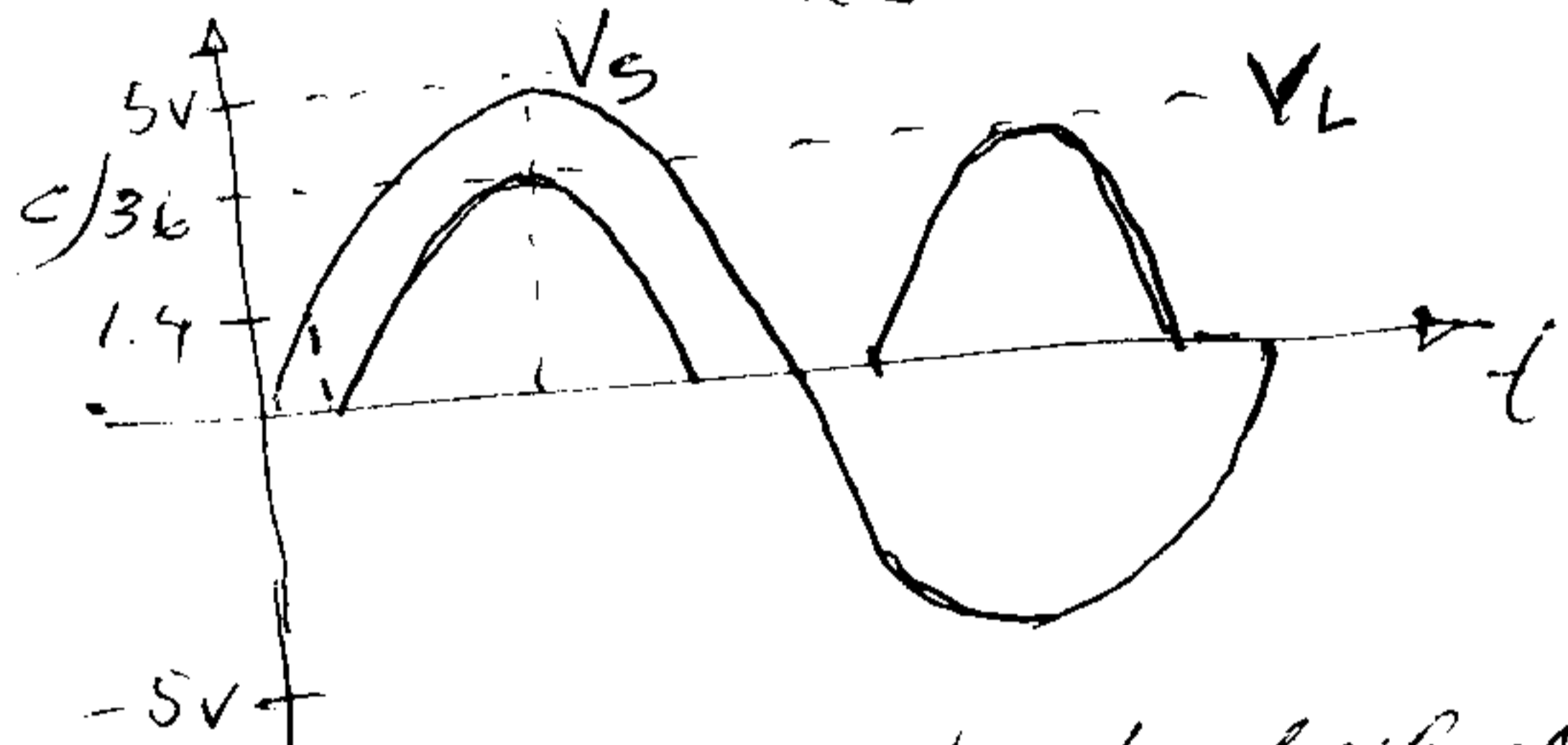


d) Tension entre $-10mV$ et $+10mV$. Toutes les diodes OFF.
 $V_L = 0V$

e) $V_s = 5V + 10 \sin(\omega t) mV$
D2, D3 sont OFF

D1, D4 sont ON

$$I_L = \frac{5 - 1.4}{R_L} = \frac{3.6}{R_L}$$
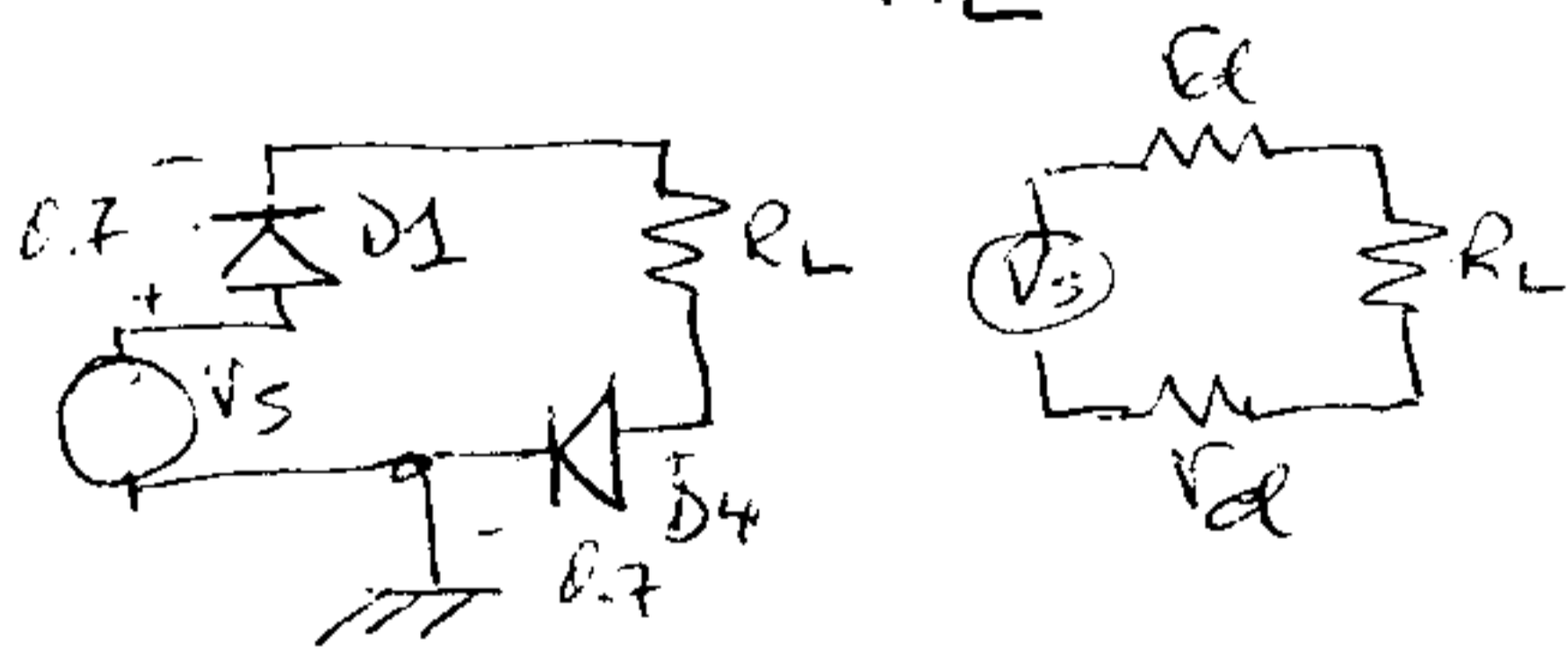
$$V_L = 3.6V \quad r_d = \frac{26mV}{I_L} = \frac{26mV}{3.6}$$



$$V_L = 3.6V + \frac{R_L}{R_L + 2r_d} \cdot 10 \sin(\omega t) mV$$

$$= 3.6V + 9.86 \sin(\omega t) mV$$

$$Q_2 - a) V_{B1} = V_{B2} = 1.8V$$


$$V_{C1} = V_{C2} = 1.8V$$

$$\bar{I}_{C1} = \bar{I}_{C2} = \frac{V_{CC} - V_{C1}}{R_1} = \frac{4 - 1.8}{R_1} = \frac{2.2}{R_1}$$

$$\bar{I}_{E1} = \bar{I}_{E2} = 1mA$$

$$\bar{I}_{C1} = \alpha \bar{I}_{E1} = \frac{100}{101} \cdot 1mA = 0.99mA$$
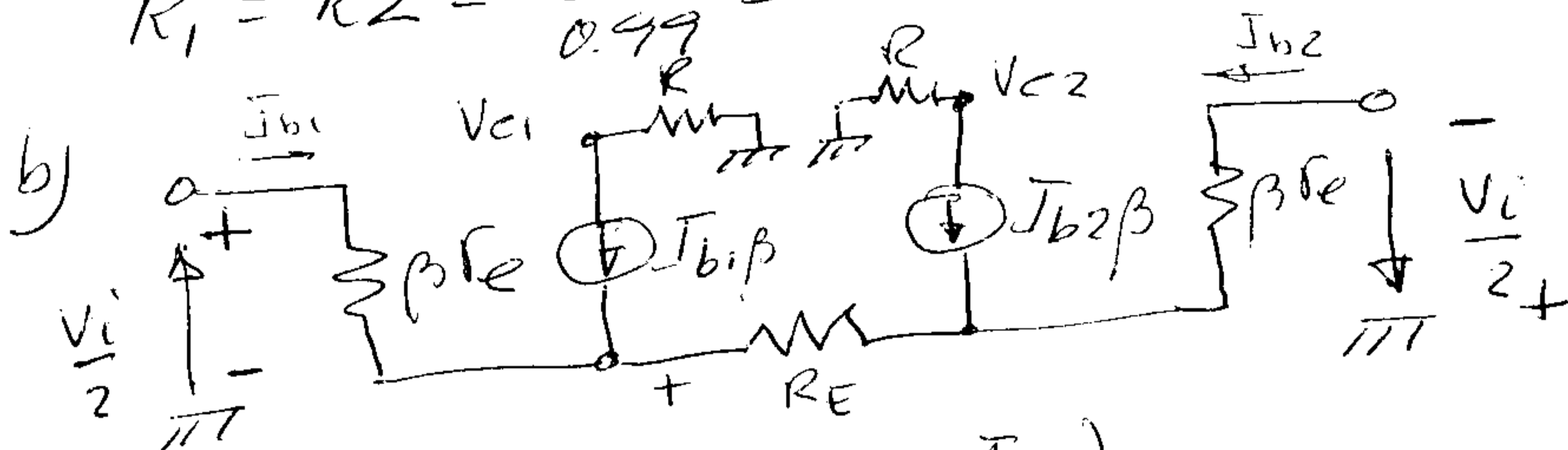
$$R_1 = R_2 = \frac{2.2}{0.99} = 2.22k\Omega$$



$$c) V_{C1} - V_{C2} = \beta R (\bar{I}_{B1} - \bar{I}_{B2})$$


$$\frac{V_i}{2} = \bar{I}_{B1} \beta r_e + V_{RE} - \bar{I}_{B2} \beta r_e - \frac{V_i}{2}$$

$$V_i = \beta r_e (\bar{I}_{B1} - \bar{I}_{B2}) + V_{RE}$$

$$V_{RE} = R_E [(\beta+1)\bar{I}_{B1} - (\beta+1)\bar{I}_{B2}] = R_E (\beta+1) (\bar{I}_{B1} - \bar{I}_{B2})$$

$$V_{C1} - V_{C2} = \frac{\beta R (\bar{I}_{B1} - \bar{I}_{B2})}{\beta r_e (\bar{I}_{B1} - \bar{I}_{B2}) + R_E [(\beta+1) (\bar{I}_{B1} - \bar{I}_{B2})]} = \frac{\beta R}{\beta r_e + (\beta+1) R_E}$$
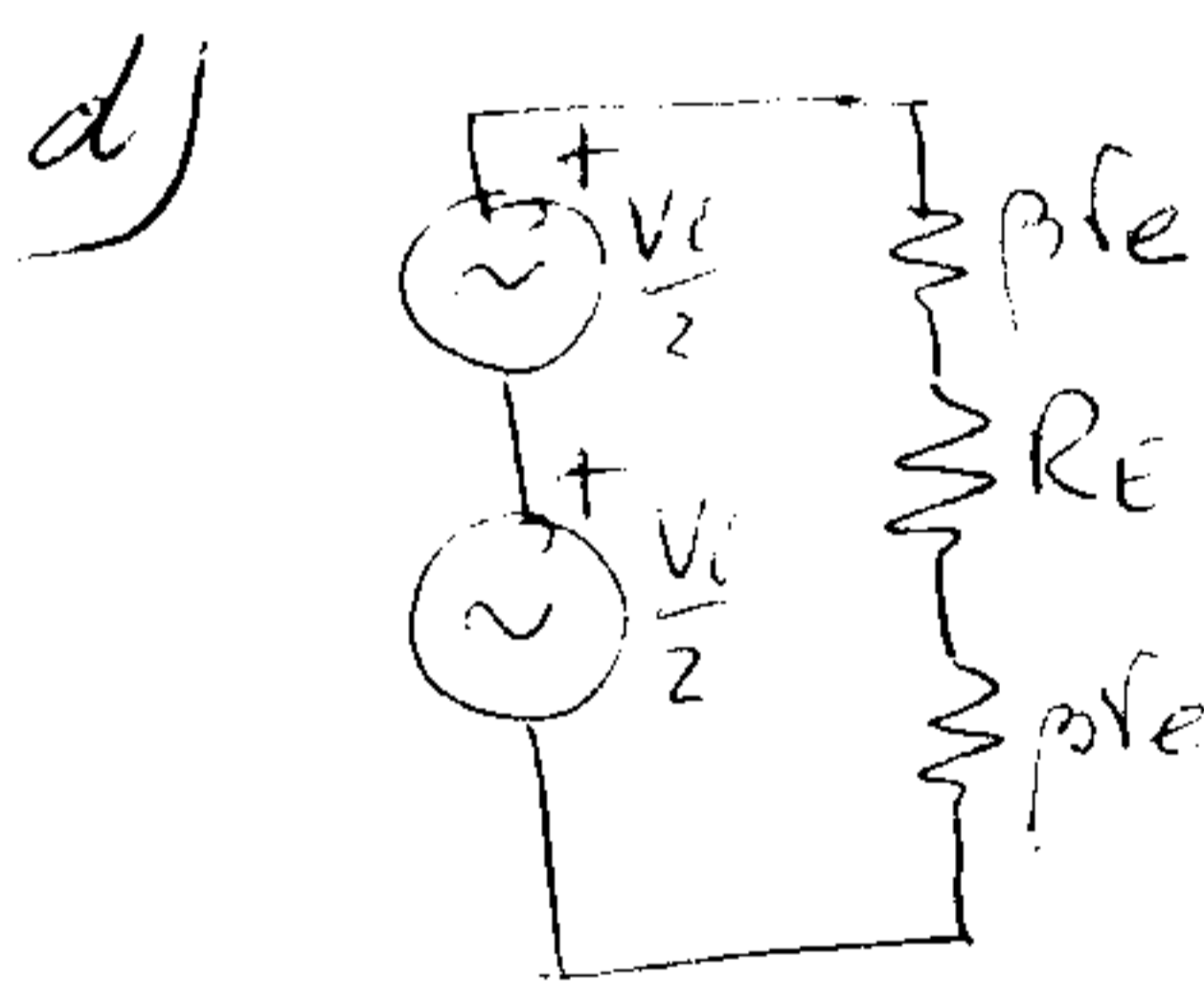
$$\frac{V_{C1} - V_{C2}}{V_i} = \frac{\beta R (\bar{I}_{B1} - \bar{I}_{B2})}{\beta r_e (\bar{I}_{B1} - \bar{I}_{B2}) + R_E [(\beta+1) (\bar{I}_{B1} - \bar{I}_{B2})]} = \frac{\beta R}{\beta r_e + (\beta+1) R_E}$$



$$R_{in} = \frac{v_{in}}{i_b} = \frac{v_{in}}{i_e} = \frac{v_{in} (\beta+1)}{i_e}$$

$$i_e = \frac{V_{RE}}{R_E} = \frac{v_{in} \frac{R_E}{2\beta r_e + R_E}}{R_E} = \frac{v_{in}}{2\beta r_e + R_E}$$

$$R_{in} = \frac{v_{in} (\beta+1)}{v_{in} \frac{(\beta+1)}{2\beta r_e + R_E}} = (\beta+1) (2\beta r_e + R_E)$$

Q3. — (Voir ch5. Ex 49-51) (et Ex 5.16)



$$V_{B1} = \frac{3.3k}{3.3k + 6.4k + 8k} \cdot 20 = 3.72V$$

$$V_{B2} = \frac{6.4k + 3.3k}{3.3k + 6.4k + 8k} \cdot 20 = 10.96V$$

$$V_{E1} = V_{B1} - 0.7 = 3.72 - 0.7 = 3.02V$$

$$I_{C1} \approx I_{E1} = \frac{V_{E1}}{R_E} = \frac{3.02}{1k} = 3mA = I_{E2} \approx I_{C2}$$
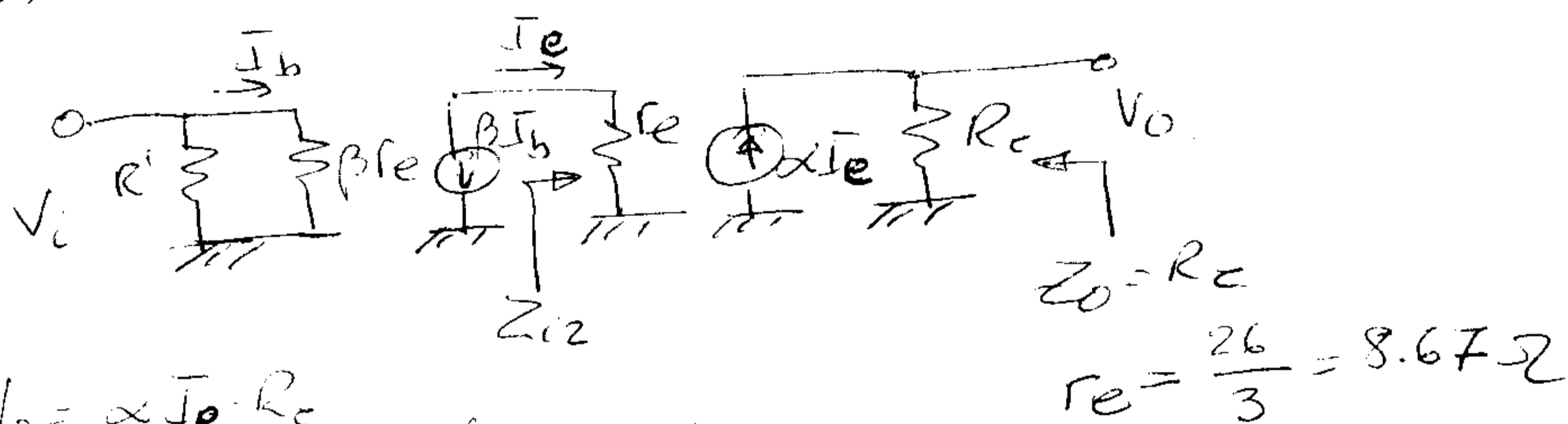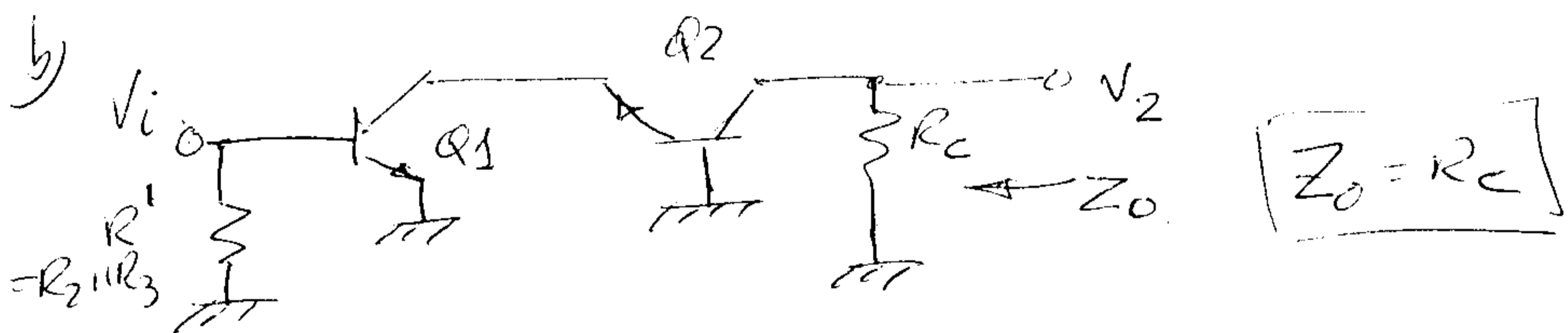
$$V_{C2} = V_{CC} - I_{C2} R_C = 20 - (3 \cdot 2) = 14V$$



$$V_o = \alpha I_e R_c$$


$$I_e = -\beta I_b = -\beta \frac{V_i}{\beta R_c} = -\frac{V_i}{R_c}$$

$$V_o = \alpha \left(-\frac{V_i}{R_c} \right) R_c$$

$$\boxed{\frac{V_o}{V_i} = -\alpha \frac{R_c}{R_c} \approx -\frac{R_c}{R_c} = -232}$$

$$r_e = \frac{26}{3} = 8.67 \Omega$$

Q4. - a)

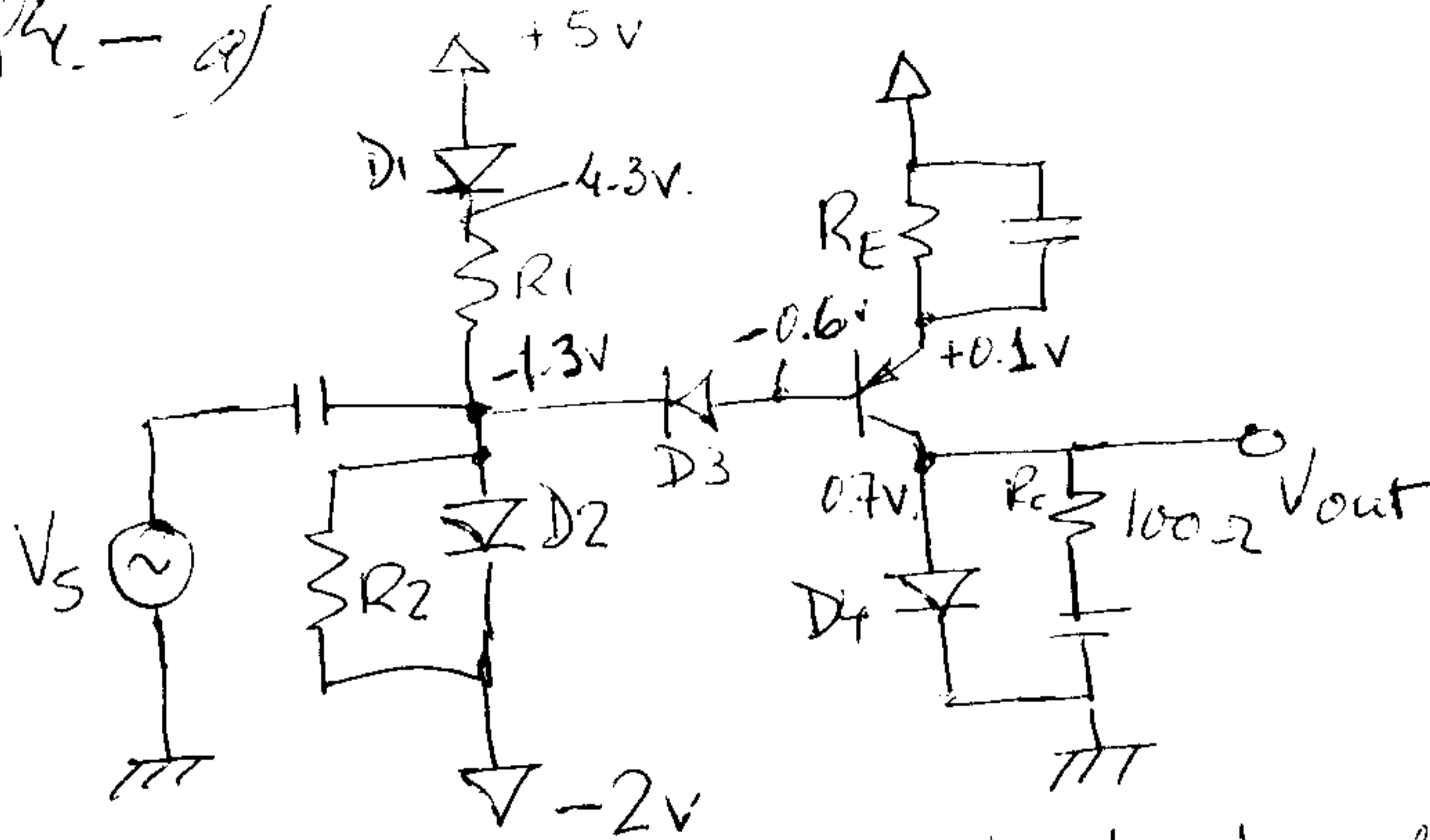

on suppose que toutes les diodes son ON


$$I_E = \frac{5 - 0.1}{980} = 5 \text{ mA} \quad I_{D4} = 2 I_E = 4.9 \text{ mA}$$

$$I_{D3} = \frac{I_C}{\beta} = 0.1 \text{ mA}$$

$$I_{D1} = \frac{4.3 - (-1.3)}{11.2 \text{ k}} = 0.5 \text{ mA} \quad I(R2) = \frac{0.7}{35 \text{ k}} = 0.2 \text{ mA}$$

$$I_{D2} = I_{D3} + I_{D1} - I(R2) = 0.4 \text{ mA}$$

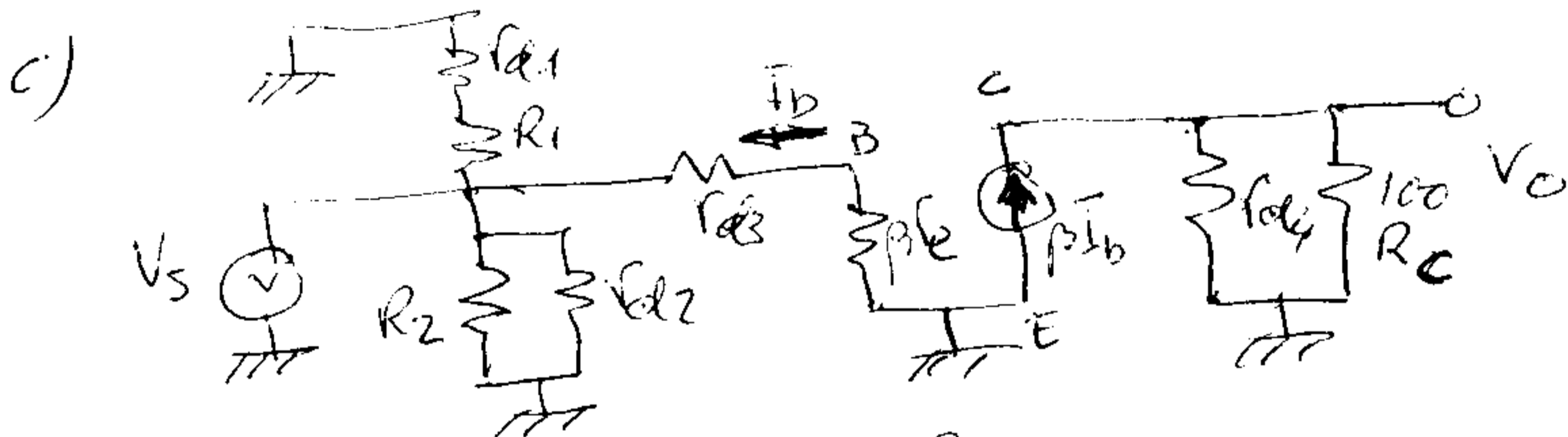b) $\frac{0.7}{R_2} \leq 0.6 \text{ mA} \quad R_2 \geq 1,167 \text{ k}\Omega$



$$r_e = \frac{26}{I_E} = \frac{26}{5.0} = 5.2 \Omega$$

$$V_o = \beta I_b (r_{d4} \parallel R_c) \quad V_s = -I_b (r_{d3} + \beta r_e)$$

par substitution

$$\frac{V_o}{V_s} = \frac{\beta (r_{d4} \parallel R_c)}{r_{d3} + \beta r_e} = \frac{50 \cdot 50}{520} = -4.8$$

$$r_{d4} = \frac{26}{4.9} = 5.3 \Omega$$

$$r_{d3} = \frac{26}{0.1} = 260 \Omega$$

$$Q5. - a) \quad 5V = V_{GS} + I_D \cdot 0.7k \quad V_G = \frac{20 \cdot 30}{170} = 5V$$

$$I_D \Big|_{V_{GS}=0} = \frac{5}{0.7k} = 7.14 \mu A = \overline{1.2 \text{ mA}}$$

$$V_{GS} \Big|_{I_D=0} = 5V = \overline{0.83 \text{ V}}$$

$$I_{DQ} = 1.1 \cdot 6 = 6.6 \text{ mA}$$

$$V_{GSQ} = 0.1 \cdot 6 = 0.6 \text{ V}$$

b)

$$\left. \begin{aligned} I_{DQ} &= I_{DSS} \left(1 - \frac{V_{GSQ}}{V_P}\right)^2 \\ 5 &= V_{GS} + I_{DQ} \cdot 0.7k \end{aligned} \right\} \begin{aligned} I_{DQ} &= 6.7 \text{ mA} \\ V_{GSQ} &= 0.31 \text{ V} \end{aligned}$$

$$c) \quad I_E = 6.7 \text{ mA} \quad I_B = \frac{I_E}{\beta+1} = \frac{6.7}{161} = \underline{\underline{41.6 \mu A}}$$

$$V_B = 20 - 330 \cdot 41.6 \cdot 10^{-3} = 6.3 \text{ V}$$

$$V_E = 5.6 \text{ V} \quad V_C = 20 - 11 \cdot 6.7 = 12.6 \text{ V}$$

$$V_{CE} = V_C - V_E = \underline{\underline{7 \text{ V}}}$$

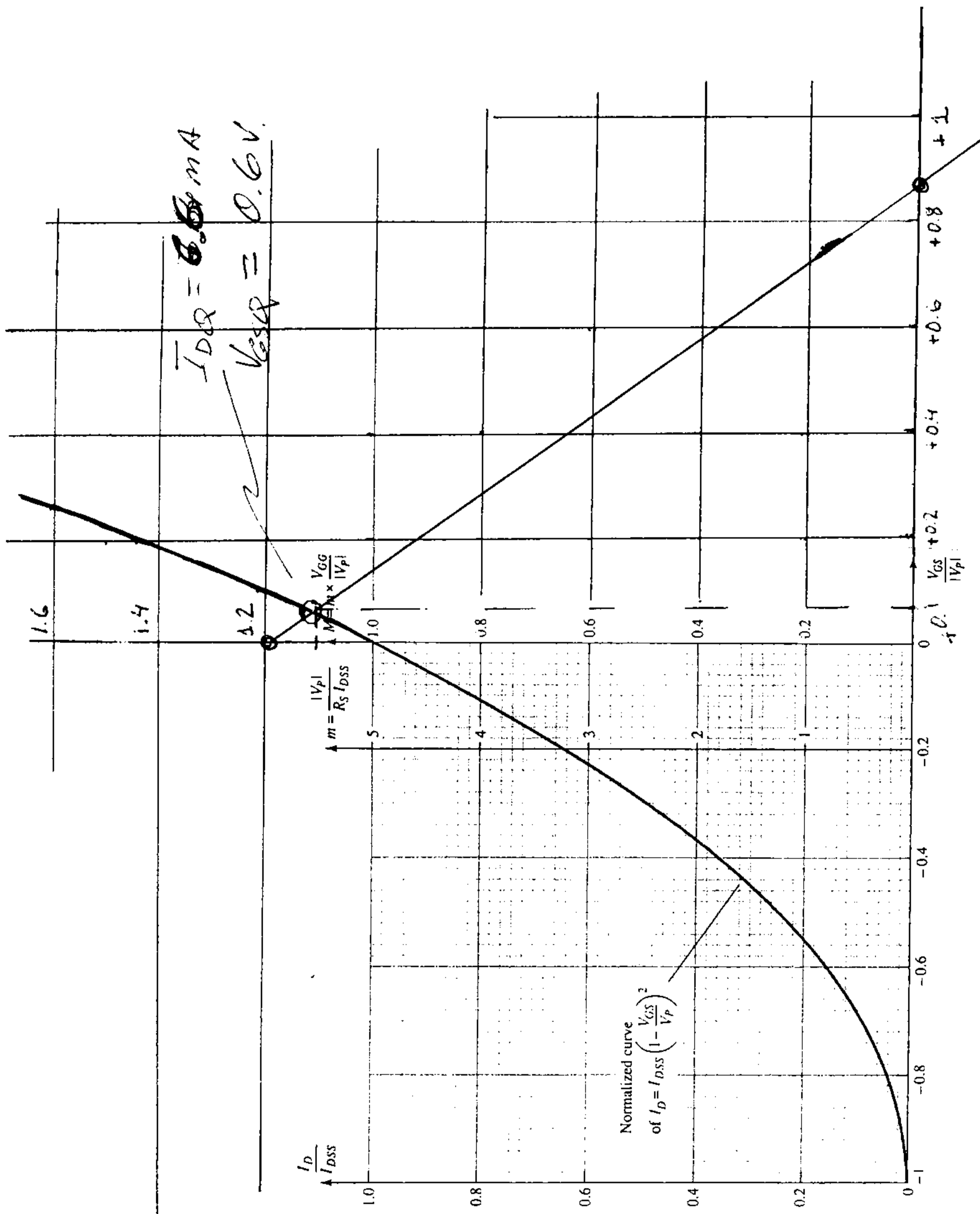


FIG. 7.60
Universal JFET bias curve.

Q6. - (Voir Ex 5.15. Problème CH 5. 47-48)


a) $\beta R_E > 10 R_2 \therefore V_B = \frac{15.8}{41} = 2.92 \text{ V}$

$V_E = 2.92 - 0.7 = 2.22$ $I_E = \frac{2.22}{1.5 \text{ k}} = 1.48 \text{ mA}$

$I_B = \frac{I_E}{\beta + 1} = \frac{1.48 \text{ mA}}{151} = 9.8 \mu\text{A}$

$I_C = \beta I_B = 150 \cdot 9.8 \cdot 10^{-3} \text{ mA} = 1.47 \text{ mA}$

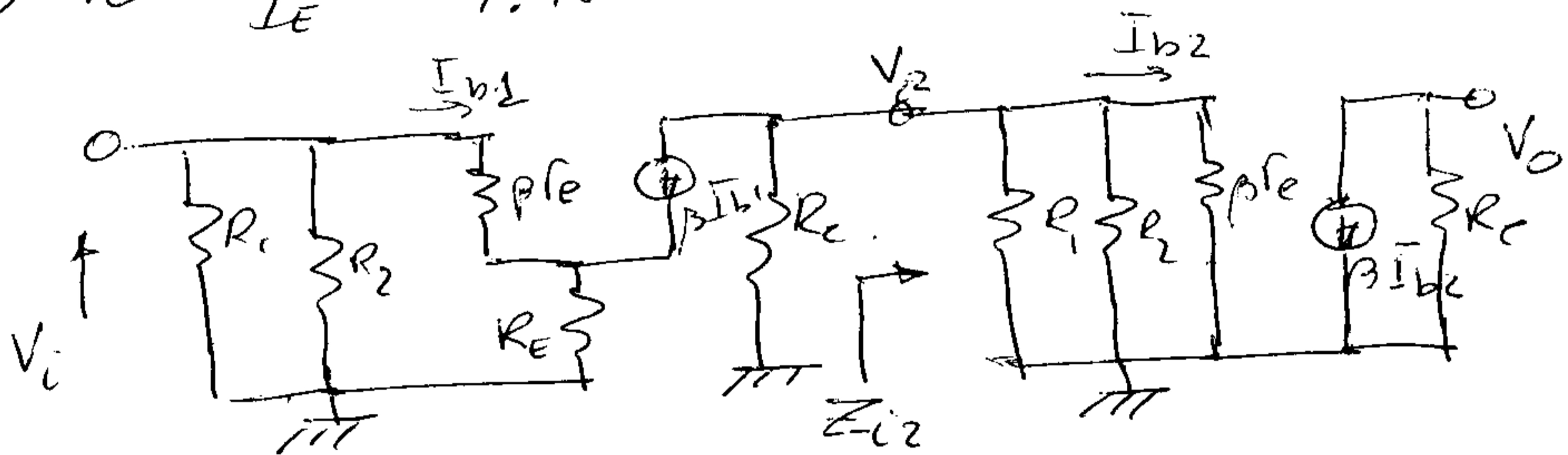b) $r_e = \frac{26 \text{ mV}}{I_E} = \frac{26}{1.48} = 17.56 \Omega$



c) $A_{V2} = \frac{V_0}{V_{i2}} = - \frac{R_c}{r_e} = - \frac{2 \text{ k}}{17.56} = -114.3$

$Z_{i2} = R_1 \parallel R_2 \parallel \beta r_{pi} = 1.8 \text{ k}$

$A_{V1} = \frac{V_{i2}}{V_i} = - \frac{R_c \parallel Z_{i2}}{r_e + R_E} = - \frac{2 \text{ k} \parallel 1.8 \text{ k}}{r_e + R_E} = -0.62$

$A_V = A_{V1} \cdot A_{V2} = 0.62 \cdot 114.3 = \underline{\underline{70.8}}$

d) $Z_i = R_1 \parallel R_2 \parallel \beta(r_e + R_E) \approx R_1 \parallel R_2 = \underline{\underline{6.22 \text{ k}\Omega}}$

$Z_o = R_c \parallel R_L = R_c = \underline{\underline{2 \text{ k}\Omega}}$