
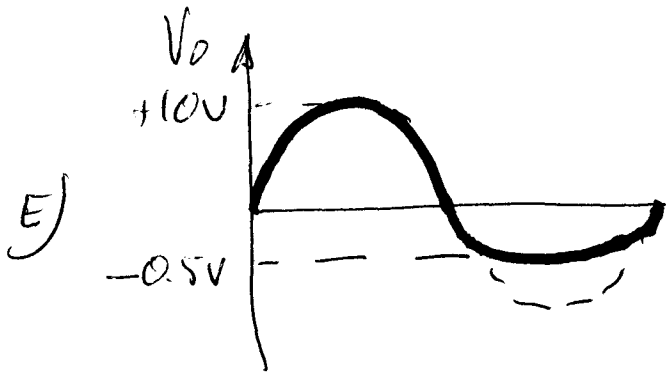
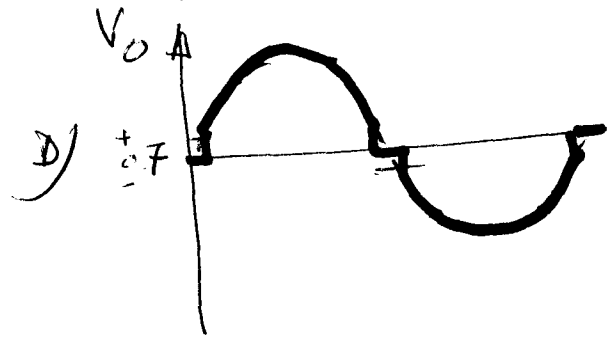
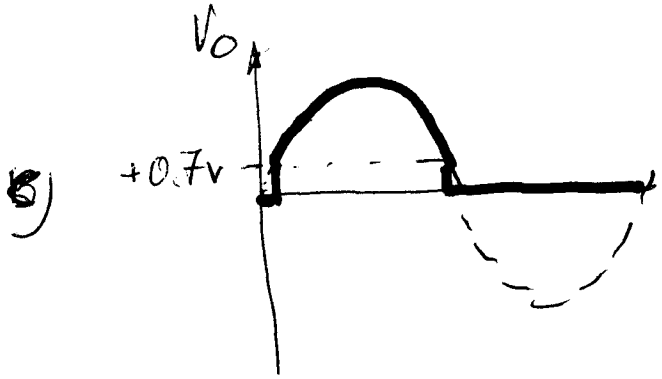
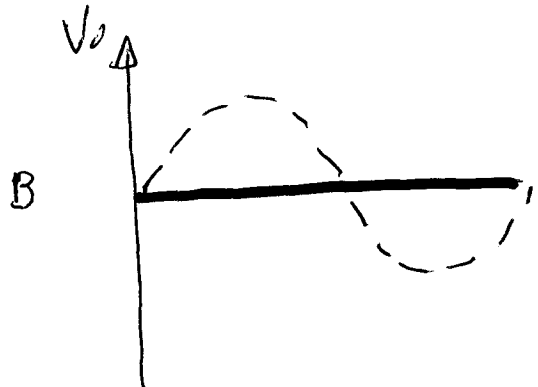


Q5.-

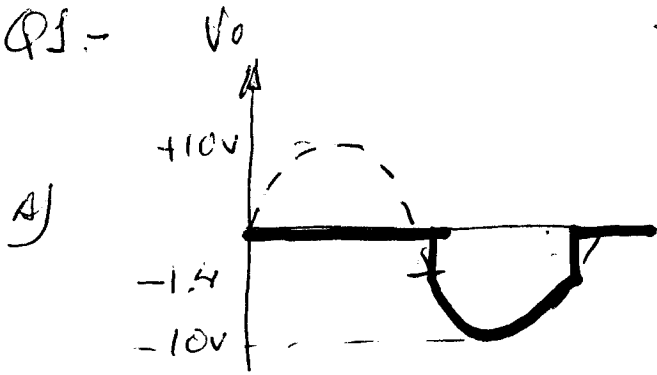


Q2.-

(2)

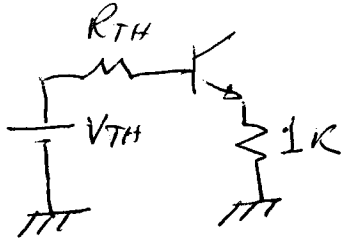a) FIG 2.  $\beta R_E \neq 10K2 \therefore V_{TH} = 20 \frac{10}{100} = 2V.$

$$R_{TH} = \frac{10 \cdot 90}{100} = 9K\Omega$$



$$2V = I_B \cdot 9K + 0.7 + I_B (\beta + 1) \cdot 1K$$

$$2 = 0.7 + I_B \cdot 50K$$

$$I_B = \frac{1.3}{50K} = 26\mu A$$


$$I_E = 41 \cdot 26\mu A = 1.07mA$$

$$I_C = \frac{40}{41} \cdot 1.07 = 1.04mA$$

$$V_1 = 20 - 1.04 \cdot 3.3 = 20 - 3.44 = 16.56V$$

$$V_2 = 0.7 + 1.07 \cdot 1K = 1.77V$$

b) FIG 3

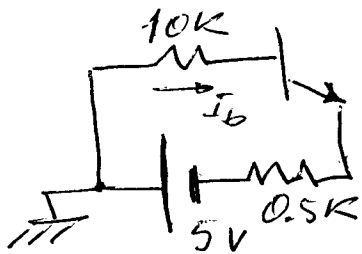

$$5 = 10K \cdot I_B + 0.7 + 41 \cdot 0.5K \cdot I_B$$


$$I_B = \frac{4.3}{30.5K} = 140\mu A$$

$$I_E = 41 \cdot 0.140 = \underline{5.7mA}$$

$$I_C = 5.6mA$$

$$V_3 = 20 - 18.3 = \underline{1.7V}$$
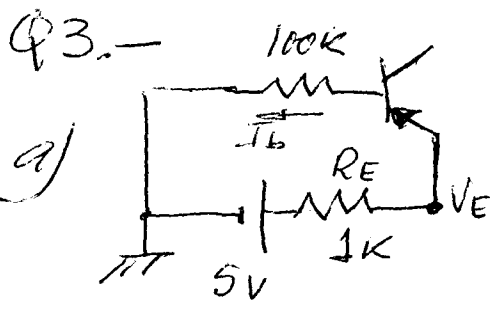
$$V_4 = 0.7 + 5.7 \cdot 0.5K = \underline{3.55V}$$



$$5V = (\beta + 1) \cdot 1k \cdot I_b + 0.7V + I_b \cdot 100k$$


$$4.3V = I_b (201 \cdot 1k + 100k) = 301k \cdot I_b$$

$$I_b = \frac{4.3}{301k} = 14 \mu A$$

$$I_c \approx I_e = 201 \cdot 14 \mu A = 2.81 mA \quad r_e = \frac{26}{2.81} = 9.2 \Omega$$

$$V_c = 5V - 2.81 \cdot 100k = 4.27V$$
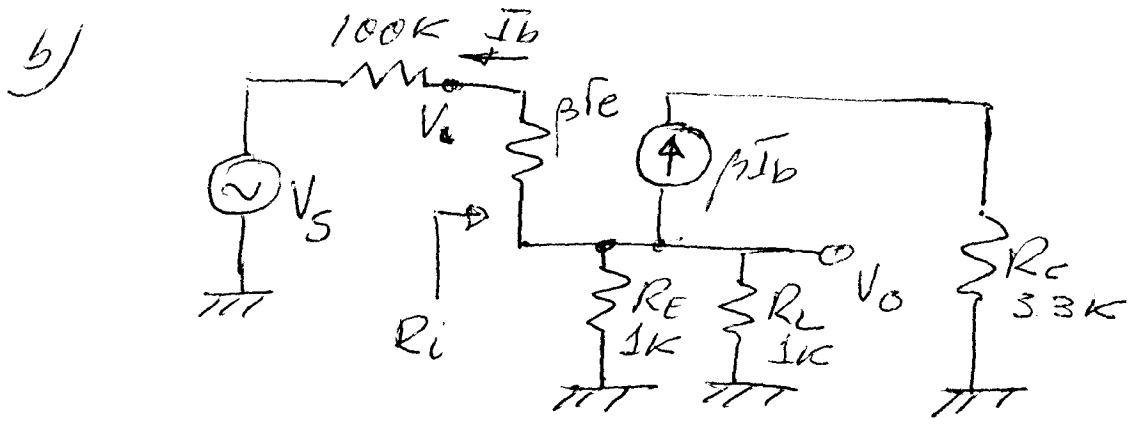
$$V_e = 5V - 2.81 \cdot 1k = \underline{\underline{2.19V}}$$



$$V_i + I_b \cdot \beta r_e = V_o$$

$$I(R_E || R_L) = (\beta + 1) I_b = - \frac{V_o}{R_E || R_L}$$

$$V_o = - (R_E || R_L) (\beta + 1) I_b$$

per substituzione

$$V_i = V_o + \frac{V_o}{(\beta + 1)(R_E || R_L)} \cdot \beta r_e$$

$$\frac{V_o}{V_i} = \frac{(\beta + 1)(R_E || R_L)}{\beta r_e + (\beta + 1)(R_E || R_L)} \approx \frac{R_E || R_L}{r_e + (R_E || R_L)}$$

$$\frac{V_o}{V_i} = \frac{0.5k}{9.2 + 0.5k} = \frac{500}{509} = \underline{\underline{0.98}}$$

Q3 (cont)

c)  $V_i = V_o - I_b \cdot \beta r_e$



$$V_i = -(R_e \parallel R_L)(\beta + 1) I_b - I_b \beta r_e$$

$$-\frac{V_i}{I_b} = R_i = \beta r_e + (\beta + 1)(R_e \parallel R_L) \approx \beta (r_e + R_e \parallel R_L)$$

$$R_i = 200(9.2 + 500) = \underline{\underline{101 \text{ k}\Omega}}$$

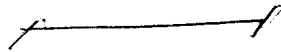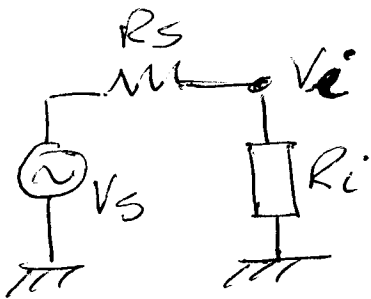
d)  $\frac{V_o}{V_s} = \frac{V_i}{V_s} \cdot \frac{V_o}{V_i} = \frac{R_i}{R_s + R_i} \cdot 0.98 = \frac{101}{201} \cdot 0.98$

$$\frac{V_o}{V_s} = \underline{\underline{0.49}}$$



Q4


5

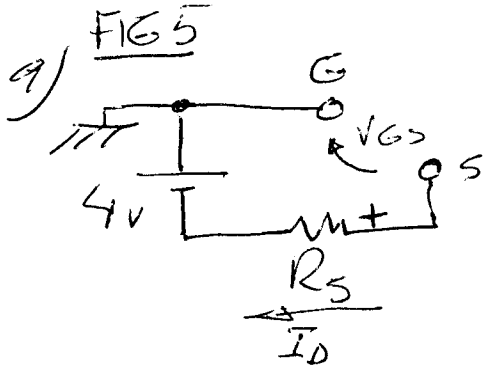

$$V_{GS} = 4 - R_S \bar{I}_D$$

$$\bar{I}_D = 8 \text{ mA} \left( 1 - \frac{V_{GS}}{-8} \right)^2$$

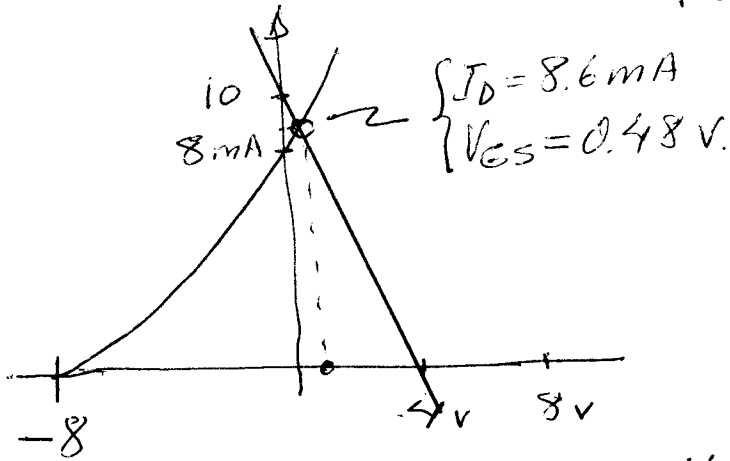Pour  $V_{GS} = 0 \rightarrow \bar{I}_D = 10 \text{ mA}$   
 $\bar{I}_D = 0 \rightarrow V_{GS} = 4$



POINT DE FONCTIONNEMENT:

$$\bar{I}_D = 8.6 \text{ mA}$$

$$V_{GS} = +0.48 \text{ V}$$

$$V_D = 18 - 8.6 \cdot 2.2 \text{ k} = -0.96 \text{ V}$$

b) FIG 6

$$V_{GS} = 0 \text{ V}$$

$$\bar{I}_D = I_{DSS} = 6 \text{ mA}$$

$$V_D = 20 - 6 \cdot 2.2 = 6.8 \text{ V}$$

