

**EXERCICES DE SIMULATION SPICE**  
**MIC4120.- SESSION HIVER 2010**

**SP1.-CIRCUIT A DIODE**

```
.model tut_diode d (is=1e-14 vj=0.6 rs=10)
vs vs gnd 5V
rs vs vd 5k
d1 vd gnd tut_diode
.dc vs 0V 5V 0.01V
.option post=2
.end
```

**SP2.- SOURCE PAR IMPULSIONS AVEC DIODE**

```
SOURCE PAR IMPULSIONS AVEC DIODE
V1 1 0 PULSE (0 10 5M 0 0 2M 4M)
R1 1 2 100
D1 2 3 DMOD
R2 3 0 1K
C1 3 0 20U
.MODEL DMOD D()
.tran 1U 20M
.PRINT TRAN V(3) V(1)
.END
```

**SP3.- RECTIF1**

```
VS1 1 0 sin(0V 168V 60)
VS2 0 3 sin(0V 168V 60)
D1 1 2 DMOD
D2 3 2 DMOD
.MODEL DMOD D()
RL 2 0 5
.tran .2m 60m
.PRINT tran V(2) V(1) i(1)
.option post
.END
```

**SP4.-FILTRE RC PASSE BAS**

```
FILTRE RC PASSE BAS
VS 1 0 AC 1 SIN(0 1 2000)
R1 1 2 1K
C1 2 0 .5U
.AC DEC 5 10 5000
.TRAN 5US 5M
* RESULTATS
.PRINT AC VM(2) VP(2)
```

```
.PLOT AC VM(2) VP(2)
.PRINT TRAN V(1) V(2)
.PLOT TRAN V(1) V(2)
.PROBE
.END
```

### **SP5.-SOURCE AC AVEC DIODE**

SOURCE AC AVEC DIODE

\*

```
VI 1 0 SIN(0 10 1KHZ)
C 1 2 10U IC=5v
D 2 3 DMOD
VB 3 0 5V
.MODEL DMOD D()
.TRAN 1U 2M UIC
.PRINT V(2)
.END
```

### **SP6.- CIRCUIT RLC**

CIRCUIT RLC

\*

```
VIN 1 0 AC 5 0
L1 2 3 0.125
C1 3 0 1U
R1 1 2 200
.AC DEC 10 1 10k
.PRINT AC IM(VIN) IP(VIN) VM(2) VP(2) VM(3) VP(3)
.PLOT AC VDB(3) VP(3)
.END
```

### **SP7.-ZENER1**

```
VS1 0 1 12
R1 1 2 5
DZ1 2 0 DMOD
.MODEL DMOD D(BV=10 IBV=100u)
RL 2 0 200
.TRAN 1U 2M
.PRINT TRAN V(2)
.END
```

### **SP8.- ZENER SPIKES**

\*

```
VS 1 0 SIN(0V 10V 1KHZ)
VP 2 1 PULSE (0V 10V 0.25M 0.01M 0.01M 1U 1M)
R 2 3 1
```

```

d1 4 3 DMOD
d2 4 0 DMOD
rl 3 0 50
.MODEL DMOD D(BV=9.3V IBV=100u)
.TRAN 1U 2M
.PRINT V(3)
.END

```

### **SP9.- ZENERLIMITTER**

```

*
Vi 1 0 DC 0V
R 1 2 1k
D1 2 0 D1N4148
D2 0 2 D1N4148
.model D1N4148 D (Is=0.1pA Rs=16 CJO=2p Tt=12n Bv=100 Ibv=0.1p)
.DC Vi -5V 5V 100mV
.PLOT DC V(2)
.PRINT V(2)
.END

```

### **SP10.- FILTRE**

```

*
VS 1 0 SIN(0 161 60)
D 1 2 DMOD
.MODEL DMOD D()
L1 2 3 0.05
C1 3 0 2000U
RL 3 0 120
.TRAN .5M 500M
.print TRAN VM(3) VM(1)
.END

```

### **SP11.- CIRCUIT DOUBLEUR DE TENSION**

```

** Circuit Description **
Vi 1 0 sin ( 0 10V 1kHz )
C1 1 2 1u
C2 3 0 1u
D1 2 0 D1N4148
D2 3 2 D1N4148
* diode model statement
.model D1N4148 D (Is=0.1pA Rs=16 CJO=2p Tt=12n Bv=100 Ibv=0.1p)

** Analysis Requests **
.TRAN 100u 10m 0m 100u
** Output Requests **
.PLOT TRAN V(1) V(2) V(3)

```

```
.probe
.end
```

### **SP12.- SOUS-CIRCUIT**

EXEMPLE DE SOUS-CIRCUIT

```
*
X1 1 2 5 INVERTER
X2 2 3 5 INVERTER
X3 3 1 5 INVERTER
VDD 5 0 5

.SUBCKT INVERTER 1 2 3
M1 2 1 0 0 ENH L=10U W=40U
M2 3 2 2 0 DEP L=10U W=5U
.MODEL DEP NMOS LEVEL=1 VTO=-3 LAMBDA=.001 KP=.4E-4
.MODEL ENH NMOS LEVEL=1 VTO=1.8 CGSO=20N LAMBDA=.001 KP=.4E-4
.ENDS INVERTER

.IC V(1)=5 V(2)=0
.TRAN .01U .5U
.PLOT TRAN V(1) V(2) V(3) (0,5)
.WIDTH OUT=80
.END
```

### **SP13.- TRANSISTOR**

```
transist2
*
vs 1 0 AC=1 sin(0v 10mV 1kHz)
CC1 1 2 100U
VEE 0 4 4
VCC 5 0 15
RE 2 4 3.3K
RC 3 5 8.1K
Q1 3 0 2 QMOD
CC2 3 6 100u
RL 6 0 15k
.MODEL QMOD NPN (Is=10fA Ikf=150mA Bf=150 Br=3 Rb=1 Va=30V)
.OP
.dc vcc 15v 15v 1v
.AC DEC 10 1 10K
.PRINT DC V(3,2)
.print ac V(3)
.TRAN 1U 1M
.measure TRAN pow FIND PAR('V(5)*I(vcc)') AT 0.2M
.print tran V(3.2)
.END
```

**SP14.- EXEMPLE DE BJT**

```
.OPTION      $ The options are listed below:
+ ingold=1   $ Use fixed-point and exponential form on output
+ numdgt=4   $ print 4 digits
```

```
*.INC /nfs/guille/analog1/m/moon/ece323/npn322.inc
```

```
Vcc  vcc  0    =12.0
q1    c    b    e    npn322
Rb1   vcc  b    2.1k
Rb2   b    0    300
Rc    vcc  c    100
Re1   e    e1   9.5
Re2   e1   0    6.5
Cout  e1   0    63u
Cin   vi   b    1u
Vin   vi   0    AC=1 SIN 0 amp 100K 0 0 180
.model npn322 npn ()
```

```
.OP
```

```
.AC DEC 10 1 1G
```

```
.NET V(c) Vin
```

```
.PRINT AC Vdb(c)
```

```
.MEASURE AC A0 FIND VR(c) AT=100K          $ Measure the gain at 10kHz.
.MEASURE AC AdB FIND VdB(c) AT=100K       $ Measure the gain at 10kHz.
.MEASURE AC mzi FIND PAR('v(vi)/i(vin)') AT=100K $ Measure the input impe
.MEASURE AC mzo FIND ZOUT(M) AT=100K      $ Measure the out. imp. @10kHz.
.MEASURE AC fl WHEN VM(c)='.707*ABS(A0)'   $ Find the lower 3dB frequency.
.MEASURE AC fu WHEN VM(c)='.707*ABS(A0)' TD=1e5 $ Find the upper 3dB frequency.
.MEASURE AC POW FIND PAR('v(vi)*i(vin)') AT 100K
```

```
.TRAN .1u 20u SWEEP amp POINTS 2 110m 500m
```

```
.PRINT TRAN V(c)
```

```
.END
```

**SP15.-CMOS AMPLIFIER**

```
* dc supplies
```

```
Vdd 1 0 DC +10V
```

```
Iref 2 0 DC 100uA
```

```

* input signal
Vi 4 0 DC 0V
* amplifier circuit
M1 3 4 0 0 nmos L=10u W=100u
M2 3 2 1 1 pmos L=10u W=100u
M3 2 2 1 1 pmos L=10u W=100u
* mosfet model statements (by default, level 1)
.model nmos nmos (kp=20u Vto=+1V lambda=0.01)
.model pmos pmos (kp=10u Vto=-1V lambda=0.01)
** Analysis Requests **
* calculate DC transfer characteristics
.DC Vi 0V +10V 10mV
** Output Requests **
.PLOT DC V(3)
.probe
.end

```

#### **SP16.- \*\* The CMOS Inverter \*\***

```

* dc supplies
Vdd 1 0 DC +5V
* input digital signal
Vi 3 0 DC +5V
* MOSFET inverter circuit
M1 2 3 0 0 MN L=3um W=3um
M2 2 3 1 1 MP L=3um W=9um
* BNR 3um transistor model statements (level 3)
.MODEL MN nmos level=3 vto=.7 kp=4.e-05 gamma=1.1 phi=.6
+ lambda=.01 rd=40 rs=40 pb=.7 cgso=3.e-10 cgdo=3.e-10
+ cgbo=5.e-10 rsh=25 cj=.00044 mj=.5 cjsw=4.e-10 mjsw=.3
+ js=1.e-05 tox=5.e-08 nsub=1.7e+16 nss=0 nfs=0 tpg=1 xj=6.e-07
+ ld=3.5e-07 uo=775 vmax=100000 theta=.11 eta=.05 kappa=1
.MODEL MP pmos level=3 vto=-.8 kp=1.2e-05 gamma=.6 phi=.6
+ lambda=.03 rd=100 rs=100 pb=.6 cgso=2.5e-10 cgdo=2.5e-10
+ cgbo=5.e-10 rsh=80 cj=.00015 mj=.6 cjsw=4.e-10 mjsw=.6
+ js=1.e-05 tox=5.e-08 nsub=5.e+15 nss=0 nfs=0 tpg=1 xj=5.e-07
+ ld=2.5e-07 uo=250 vmax=70000 theta=.13 eta=.3 kappa=1
** Analysis Requests **
.DC Vi 0 5 50mV
** Output Requests **
.PLOT DC V(2) Id(M1)
.probe
.end

```

#### **SP17.- \*\* A Simple Operational Amplifier \*\***

```

* store the simulation results requested in a graph data file
.options post

```

```

** Circuit Description **
* power supplies
Vcc 4 0 DC +15V
Vee 5 0 DC -15V
* differential-mode signal level
Vd 101 0 DC 0V
* for small-signal parameters, bias with -Vos across input terminals
* Vd 101 0 DC -178.5uV AC 1
Rd 101 0 1
EV+ 1 100 101 0 +0.5
EV- 2 100 101 0 -0.5
* common-mode signal level
Vcm 100 0 DC 0V
* 1st stage
R1 4 7 20k
R2 4 8 20k
Q1 7 1 6 npn_transistor
Q2 8 2 6 npn_transistor
Q3 6 9 5 npn_transistor
* 2nd stage
R3 4 11 3k
Q4 4 7 10 npn_transistor
Q5 11 8 10 npn_transistor
Q6 10 9 5 npn_transistor 4
* 3rd or output stage
R4 4 12 2.3k
Q7 13 11 12 pnp_transistor
R5 13 5 15.7k
Q8 4 13 3 npn_transistor
R6 3 5 3k
* biasing stage
Rb 0 9 28.6k
Q9 9 9 5 npn_transistor
* transistor model statements
.model npn_transistor npn ( Is=1.8fA Bf=100 Vaf=100V )
.model pnp_transistor pnp ( Is=1.8fA Bf=100 Vaf=100V )
** Analysis Requests **
* compute DC operating point using the following initial guesses
.OP
.NODESET V(3)=0V V(6)=-0.7V V(7)=+10V V(8)=+10V V(9)=-14.3V V(10)=+9.3V
+ V(11)=+12V V(12)=+12.7V V(13)=+0.7V
* compute large-signal differential-input transfer characteristics of amp
.DC Vd -15V +15V 100mV
* expanded view of high-gain region
* .DC Vd -5mV +5mV 10uV
** Output Requests **
.PLOT DC V(3)

```

```

* compute the small-signal parameters of the amplifier
* .tf v(3) vd
* .ac lin 1 1Hz 1Hz
* .print ac Im(ev+) Im(ev-) vm(1,2)
* for input common-mode range (with Vd=-178.5uV)
* .DC Vcm -15V +15V 0.1V
.end

```

### **SP18.- \*\* A Common-Emitter Amplifier \*\***

```

* power supplies
Vcc 1 0 DC +12V
* input signal source
Vs 7 0 AC 1V
Rs 7 6 4k
* CE stage
Cc1 6 3 1uF
R1 1 3 8k
R2 3 0 4k
Q1 2 3 4 Q2N3904
Re 4 0 3.3k
Rc 1 2 6k
Ce 4 0 10uF
Cc2 2 5 1uF
* output load
Rl 5 0 4k
*
* transistor model statement for 2N3904
.model Q2N3904 NPN (Is=6.734f Xti=3 Eg=1.11 Vaf=74.03 Bf=416.4 Ne=1.259
+ Ise=6.734f Ikf=66.78m Xtb=1.5 Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1
+ Cjc=3.638p Mjc=.3085 Vjc=.75 Fc=.5 Cje=4.493p Mje=.2593 Vje=.75
+ Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10)
** Analysis Requests **
.OP
.AC DEC 10 1Hz 100MegHz
** Output Requests **
.PLOT AC VdB(5)
.probe
.end

```

### **SP19.- \*\* A Cascode Amplifier \*\***

```

* power supplies
Vcc 1 0 DC +15V
* input signal source
Vs 9 0 AC 1V
Rs 9 8 4k

```



```

* CE stage (input stage)
Cc1 6 8 1uF
R1 1 3 18k
R2 3 6 4k
R3 6 0 8k
Q1 4 6 7 Q2N3904
Re 7 0 3.3k
Ce 7 0 10uF
* CB stage (upper stage)
Q2 2 3 4 Q2N3904
Rc 1 2 6k
Cb 3 0 10uF
Cc2 2 5 1uF
* output load
Rl 5 0 4k
*
* transistor model statement for 2N3904
.model Q2N3904 NPN (Is=6.734f Xti=3 Eg=1.11 Vaf=74.03 Bf=416.4 Ne=1.259
+ Ise=6.734f Ikf=66.78m Xtb=1.5 Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1
+ Cjc=3.638p Mjc=.3085 Vjc=.75 Fc=.5 Cje=4.493p Mje=.2593 Vje=.75
+ Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10)
** Analysis Requests **
.OP
.AC DEC 10 1Hz 100MegHz
** Output Requests **
.PLOT AC VdB(5)
.probe
.end

```

### **SP20- \*\* Differential Amplifier With Emitter Resistors \*\***

```

* set acout=0 so HSPICE calculates vdb(x,y) as "magnitude of difference",
* rather than "difference of magnitude"
.options post acout=0

** Circuit Description **
* power supplies
Vcc 1 0 DC +10V
* input signal source
Vs 6 0 AC 1V
Rs 6 5 5k
* differential pair
Rc1 1 2 10k
Rc2 1 3 10k
Q1 3 5 7 Q2N3904

```

```

Q2 2 77 8 Q2N3904
Rs2 77 0 5k
* emitter resistors
* zero-resistance
Re1 7 4 0.00001
Re2 8 4 0.00001
* current biasing
Ibias 4 0 1mA
*
* transistor model statement for 2N3904
.model Q2N3904 NPN (Is=6.734f Xti=3 Eg=1.11 Vaf=74.03 Bf=416.4 Ne=1.259
+ Ise=6.734f Ikf=66.78m Xtb=1.5 Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1
+ Cjc=3.638p Mjc=.3085 Vjc=.75 Fc=.5 Cje=4.493p Mje=.2593 Vje=.75
+ Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10)
** Analysis Requests **
.OP
.ac DEC 10 1Hz 100MegHz
** Output Requests **
.print vdb(3,2)

* re-run simulation for resistor values 100, 200 and 300
.alter
Re1 7 4 100
Re2 8 4 100

.alter
Re1 7 4 200
Re2 8 4 200

.alter
Re1 7 4 300
Re2 8 4 300
.end

```

### **SP21.- CE AMPLIFIER**

```

* VS 1 0 AC 5 0
vs 1 0 sin(0v 4v 10k)
RS 1 2 100K
CC1 2 3 100U
Q1 4 3 0 QNPN
RF 3 4 180K
RC 4 5 2K
VCC 5 0 12V
CC2 4 6 100U
RL 6 0 2K
.MODEL QNPN NPN()
.DC VCC 12V 12V 1V

```

```

*.AC DEC 10 1 10K
*.PRINT AC IM(VS) IP(VS) V(3) V(4)
.TRAN 1U .1M
.PRINT DC V(3) V(4)
*.PLOT AC VDB(3) VP(3)
.print tran V(3) V(4) IM(VS)
*.probe
.END

```

### SP22.- \*\* Common-Emitter Amplifier Stage \*\*

```

** HSPICE Circuit Description **
* power supplies
Vcc 1 0 DC +10V
Vee 8 0 DC -10V
* input signal
* for output resistance, change Vs from 10mV to 0V
Vs 6 0 AC 10mV
Rs 5 6 10k
* amplifier
C1 4 5 1GF
Rb 4 0 100k
XQ1 2 4 3 t2n2222a
Rc 1 2 10k
Re 3 8 10k
C2 2 7 1GF
C3 3 10 1GF
* emitter degeneration resistor (vary as needed)
Rdegen 10 0 100
* load + ammeter
Rl 7 9 10k
* for output resistance, change Vout from 0 to 10mV
* Vout 9 0 AC 10mV
Vout 9 0 0
* HSpice transistor model statement for the 2N2222A
* betaf=100 in this example: also vary to 153 and 200
.macro t2n2222a 1 2 3 betaf=100 tauf=5.1e-10
*02-870918
q2n2222a 1 2 3 t2n2222a
.model t2n2222a npn
+ iss = 0.   xtf = 1.   ns = 1.00000
+ cjs = 0.   vjs = 0.50000 ptf = 0.
+ mjs = 0.   eg = 1.10000 af = 1.
+ itf = 0.50000 vtf = 1.00000 bf = betaf
+ br = 40.00000 is = 1.6339e-14 vaf = 103.40529
+ var = 17.77498 ikf = 1.00000 ise = 4.6956e-15

```

```
+ ne = 1.31919 ikr = 1.00000 isc = 3.6856e-13
+ nc = 1.10024 irb = 4.3646e-05 nf = 1.00531
+ nr = 1.00688 rbm = 1.0000e-02 rb = 71.82988
+ rc = 0.42753 re = 3.0503e-03 mje = 0.32339
+ mjc = 0.34700 vje = 0.67373 vjc = 0.47372
+ tf = tauf tr = 380.00e-9 cje = 2.6734e-11
+ cjc = 1.4040e-11 fc = 0.95000 xcjc = 0.94518
+ subs = 1
.eom
** Analysis Requests **
* calculate DC bias point information
.OP
.AC LIN 10 .5kHz 10kHz
** Output Requests **
* voltage gain  $A_v=V_o/V_s$ 
.PRINT AC Vm(6) Vp(6) Vm(7) Vp(7)
* current gain  $A_i=I_o/I_i$ 
.PRINT AC Im(Vs) Ip(Vs) Im(Vout) Ip(Vout)
* input resistance  $R_i=V_i/I_i$ 
.PRINT AC Vm(4) Vp(4) Im(Vs) Ip(Vs)
* for output resistance, print these values too
* .PRINT AC Vm(7) Vp(7) Im(Vout) Ip(Vout)
.end
```