
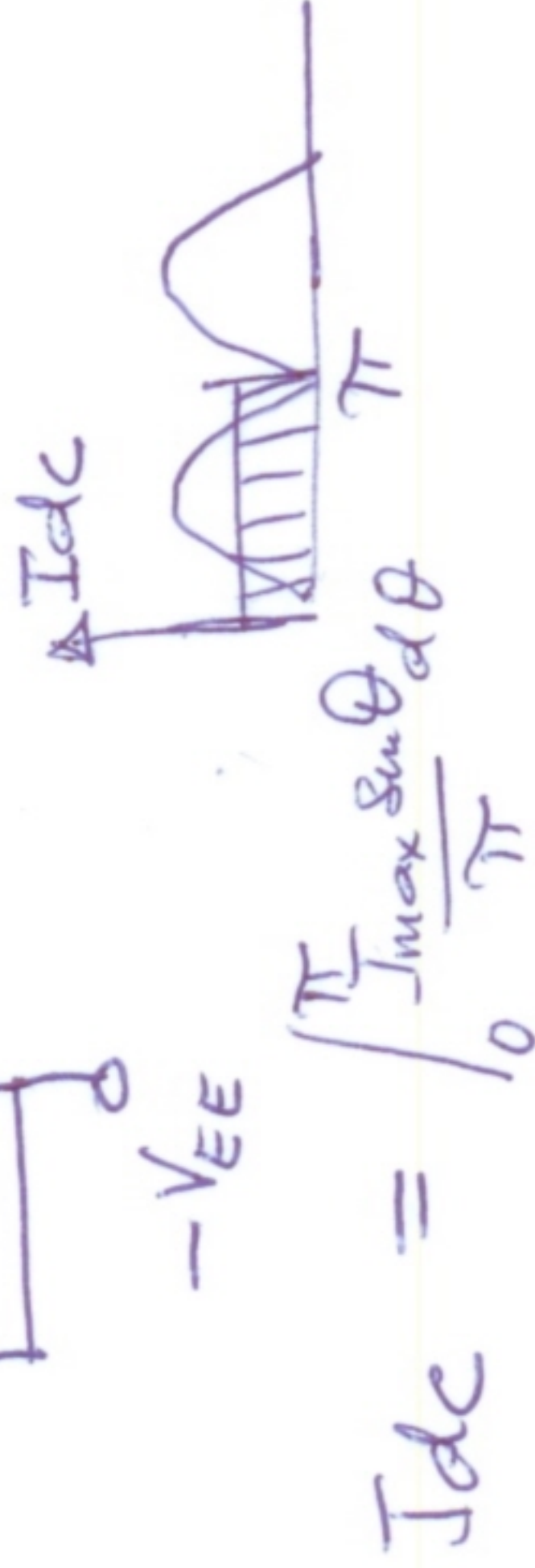
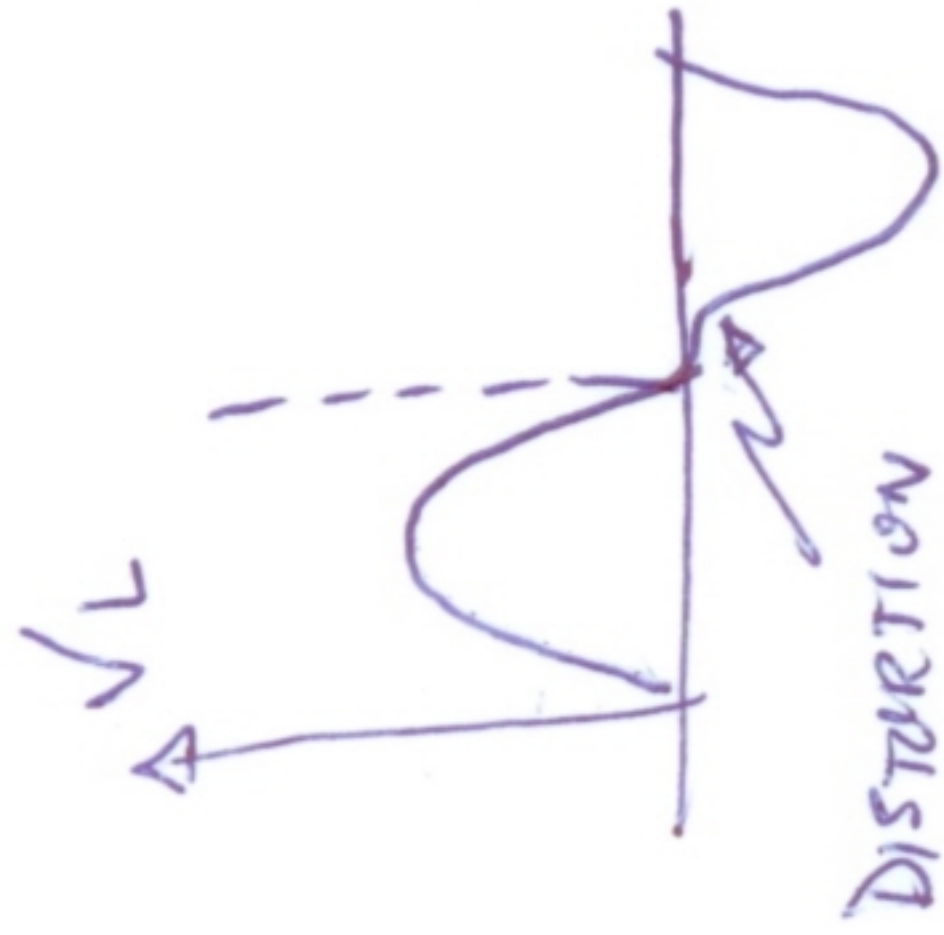


# AMPLIF CLASSE B

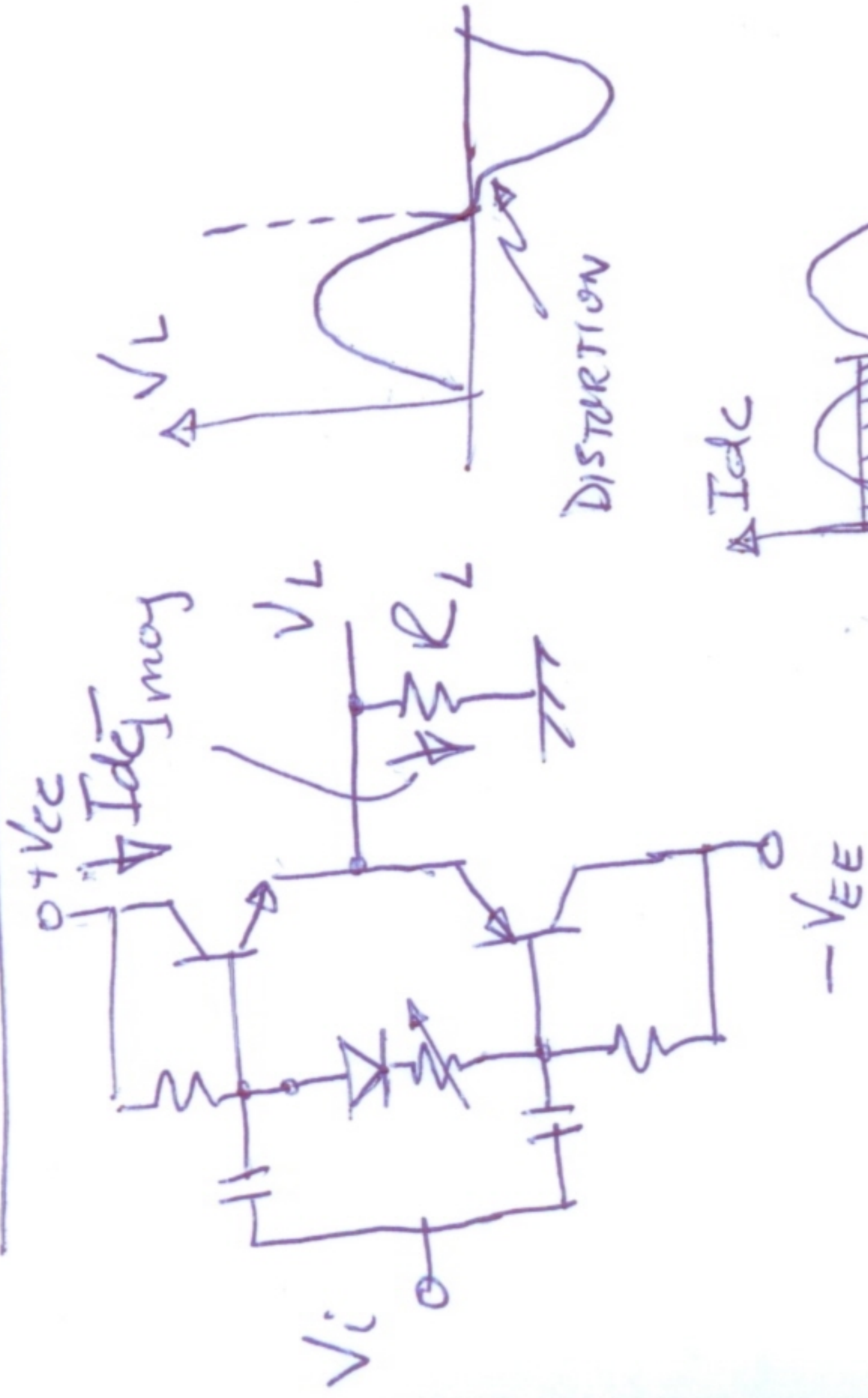

$$I_{dc} = \int_0^{\pi} \frac{I_{max} \sin \theta}{\pi} d\theta$$

$$I_{dc} = \frac{I_{max}}{\pi} \left[ -\cos \theta \right]_0^{\pi} = \frac{2 I_{max}}{\pi}$$

$$P_i(dc) = V_{cc} \frac{2 I(P)}{\pi}$$

$$P_o(ac) = \frac{V_L^2(rms)}{R_L} = \frac{V_L^2(P)}{2 R_L}$$

RENDMENT

$$\eta \% = \frac{P_o(ac)}{P_i(dc)} = \frac{\pi}{4} \frac{V_L(P)}{V_{cc}} \%$$

$$MAX = \eta = \frac{\pi}{4} = 78.5\%$$

# DISSIPATION DES TRANSISTORS


$$P_D = P_i(dc) - P_o(ac) =$$

$$P_D = \frac{2}{\pi} V_L V_{cc} - \frac{1}{2} \frac{V_L^2}{R_L}$$

TENSION  $V_L$  DE DISSIPATION MAXIMUM

$$\frac{dP_D}{dV_L} = 0 = \frac{2}{\pi} \frac{V_{cc}}{R_L} - \frac{2}{2} \frac{V_L}{R_L}$$

$$V_o = \frac{2}{\pi} V_{cc}$$

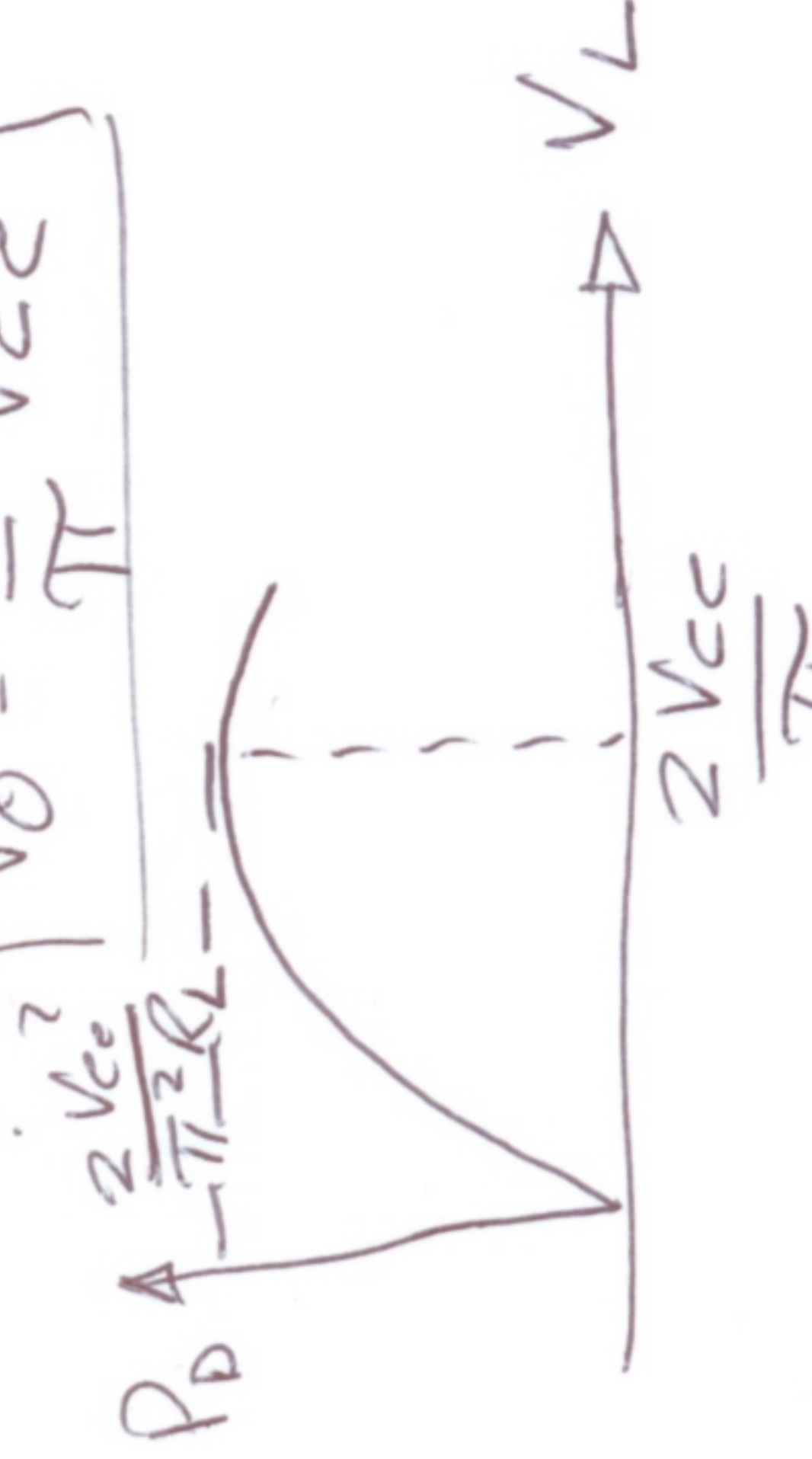

ON PEUT OBTENIR LA PUISSANCE DE DISSIPATION MAXIMALE

$$P_D(max) = \frac{2 V_{cc}^2}{\pi^2 R_L}$$

AMPLI PUISSANCE CLASSE A


$V_{CC}$

$R_B$   $R_E = \text{charge}$

$$P_{i(dc)} = V_{CC} \cdot I_C$$

$$P_{o(ac)} = \frac{V_c^2 (rms)}{R_c}$$
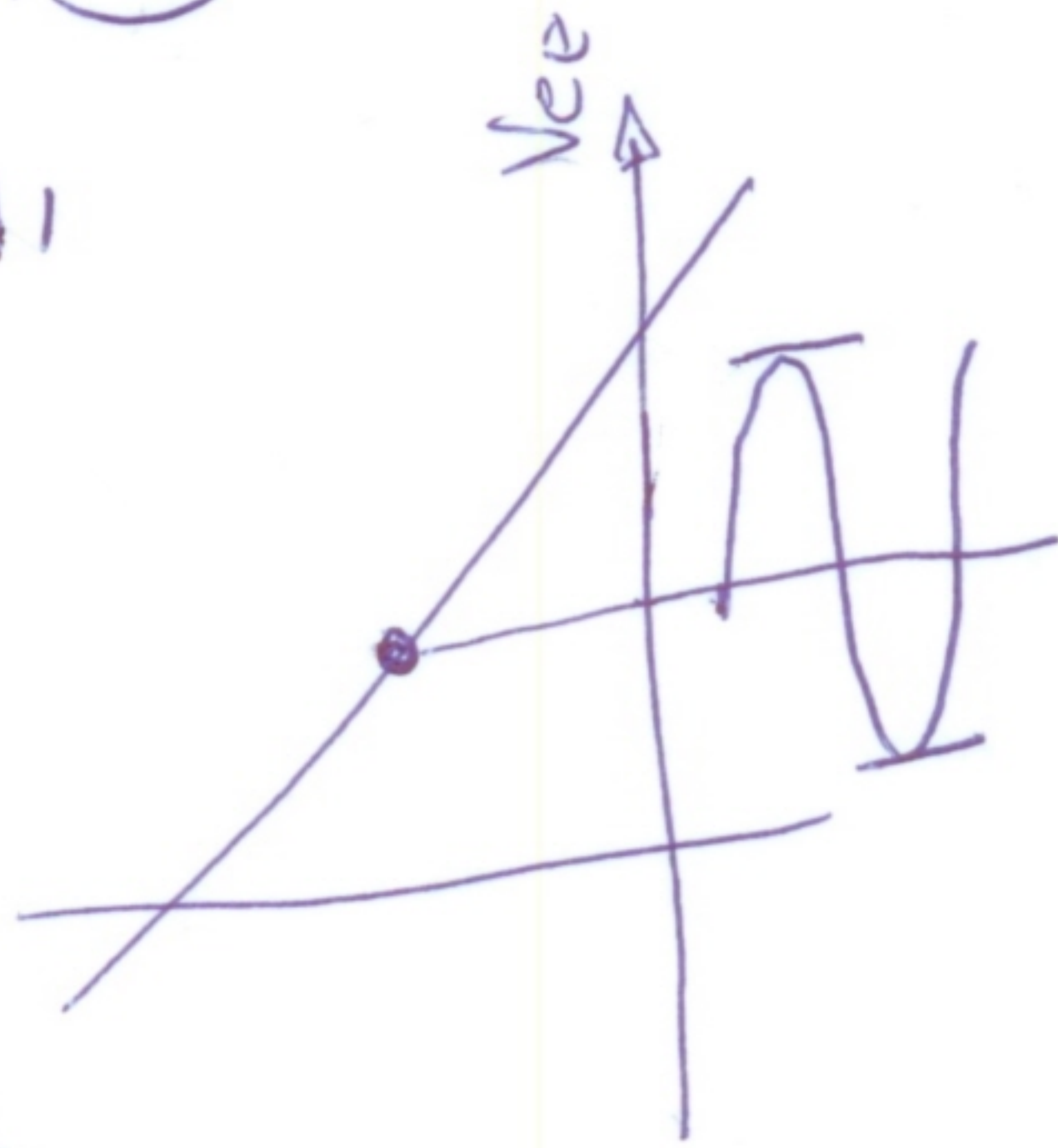
$$= \frac{V_{CE}^2 (P-P)}{(2\sqrt{2})^2 \cdot R_c} = \frac{2}{8} \frac{V_{CE}^2 (P-P)}{R_c}$$



RENDEMENT


$$\eta(\%) = \frac{P_{o(ac)}}{P_{i(dc)}} \times 100$$

$$\text{MAX } P_{i(dc)} = V_{CC} \cdot \frac{V_{CC}}{2R_c}$$

$$\text{MAX } P_{o(ac)} = \frac{V_{CC}^2}{8R_c}$$

$$\text{RENDEMENT MAXIMUM} = \frac{\text{MAX } P_{o(ac)}}{\text{MAX } P_{i(dc)}} = \frac{1}{4} = 25\%$$

RELIÉ PAR TRANSFO

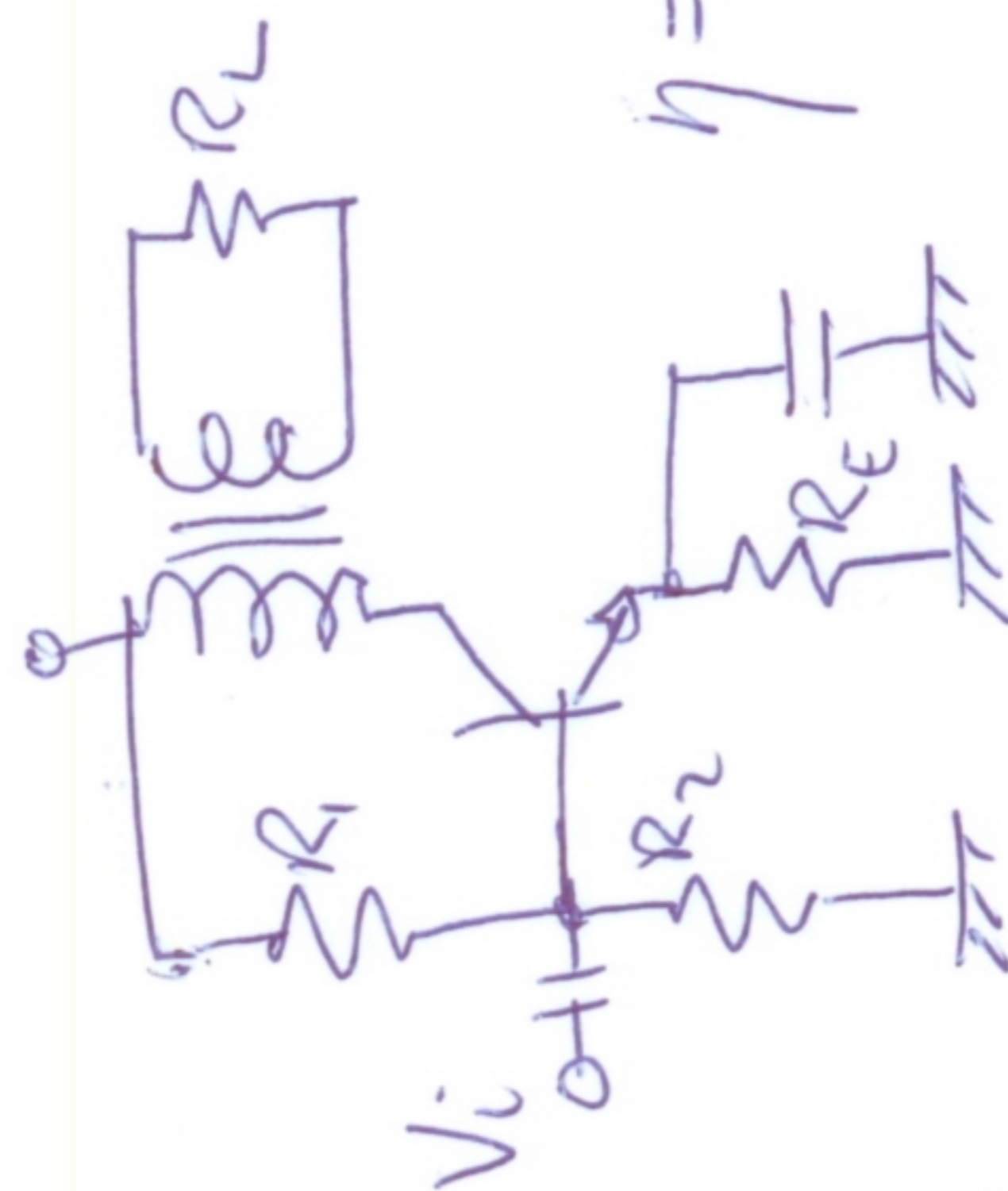

$I_{CQ} = 140mA$

$$\eta = 50 \left( \frac{V_{CEMAX} - V_{CEMIN}}{V_{CEMAX} + V_{CEMIN}} \right)^2 \%$$